

Gate EE-2015 SET-1


AI24BTECH11032 Shreyansh Sonkar

- 1) A random variable X has probability density function $f(x)$ as given below:

$$f(x) = \begin{cases} a + bx & \text{if } 0 < x < 1, \\ 0 & \text{otherwise} \end{cases}$$


If the expected value $E[X] = \frac{2}{3}$, then $\Pr[X < 0.5]$ is

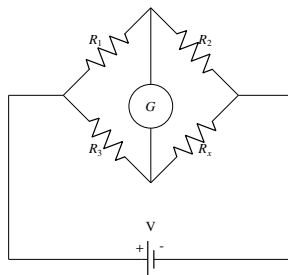- 2) If a continuous function $f(x)$ does not have a root in the interval $[a, b]$ then which one of the following statements is TRUE?
- $f(a) \cdot f(b) = 0$
 - $f(a) \cdot f(b) < 0$
 - $f(a) \cdot f(b) > 0$
 - $\frac{f(a)}{f(b)} \leq 0$
- 3) If the sum of the diagonal elements of a 2×2 matrix is -6 , then the maximum possible value of determinant of the matrix is _____.
- 4) Consider a function $\vec{f} = \frac{1}{r^2} \hat{r}$ where r is the distance from the origin and \hat{r} is the unit vector in the radial direction. The divergence of this function over a sphere of radius R , which includes the origin, is
- 0
 - 2π
 - 4π
 - $R\pi$
- 5) When the Wheatstone bridge shown in the figure is used to find the value of resistor R_X , the galvanometer G indicates zero current when $R_1 = 50\Omega$, $R_2 = 65\Omega$ and $R_3 = 100\Omega$. If R_3 is known with $\pm 5\%$ tolerance on its nominal value of 100Ω , what is the range of R_X in Ohms ?





- a) [123.50, 136.50]
- b) [125.89, 134.12]
- c) [117.00, 143.00]
- d) [120.25, 139.75]

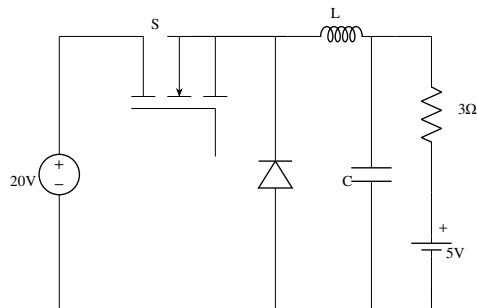
- 6) A (0 – 50A) moving coil ammeter has a voltage drop of 0.1V V across its terminals at full scale deflection. The external shunt resistance (in milliohms) needed to extend its range to (0 – 50A) is _____.
- 7) Of the four characteristics given below, which are the major requirements for an instrumentation amplifier?
- P. High common mode rejection ratio
 - Q. High input impedance
 - R. High linearity
 - S. High output impedance
- a) P, Q and R only
 - b) P and R only
 - c) P, Q and S only
 - d) Q, R and S only
- 8) In the following chopper, the duty ratio of switch S is 0.4. If the inductor and capacitor are sufficiently large to ensure continuous inductor current and ripple free capacitor voltage, the charging current (in Ampere) of the 5V battery, under steady-state, is _____.



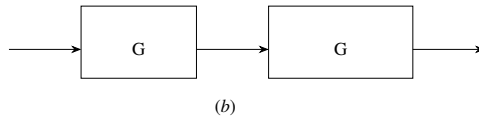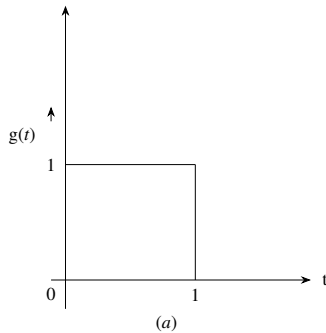
- 9) A moving average function is given by $y(t) = \frac{1}{T} \int_{t-T}^t u(\tau) d\tau$. If the input u is a sinusoidal signal of frequency $\frac{1}{2T}$ Hz, then in steady state, the output y will lag u (n degree) by _____.
- 10) The impulse response $g(t)$ of a system, G , is as shown in Figure (a). What is the maximum value attained by the impulse response of two cascaded blocks of G as shown in Figure (b) ?



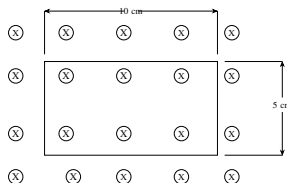- a) $\frac{2}{3}$ b) $\frac{3}{4}$ c) $\frac{4}{5}$ d) 1
- 11) Consider a one-turn rectangular loop of wire placed in a uniform magnetic field as shown in the figure. The plane of the loop is perpendicular to the field lines. The resistance of the loop is 0.4Ω , and its inductance is negligible. The magnetic flux density (in Tesla) is a function of time, and is given by $B(t) = 0.25 \sin \omega t$, where $\omega = 2\pi \times 50 \frac{\text{radian}}{\text{second}}$. The power absorbed (n Watt) by the loop from the magnetic field is _____.



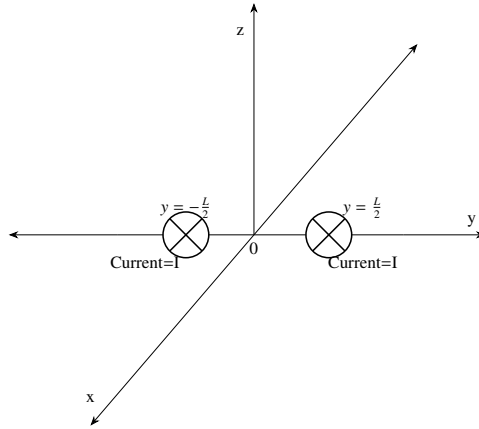- 12) A steady current I is flowing in the $-x$ direction through each of two infinitely long wires at $y = \pm \frac{L}{2}$ as shown in the figure. The permeability of the medium is μ_0 . The \vec{B} -field at $(0, L, 0)$ is



- a) $-\frac{4\mu_0 I}{3\pi L} \hat{z}$ b) $+\frac{4\mu_0 I}{3\pi L} \hat{z}$ c) 0 d) $-\frac{3\mu_0 I}{4\pi L} \hat{z}$
- 13) Consider the circuit shown in the figure. In this circuit $R = 1\text{k}\Omega$, and $C = 1\mu\text{F}$. The input voltage is sinusoidal with a frequency of 50Hz, represented as a phasor with magnitude V_i and phase angle 0 radian as shown in the figure. The output voltage is represented as a phasor with magnitude V_o and phase angle δ radian. What is the value of the output phase angle δ (in radian) relative to the phase angle of the input voltage?

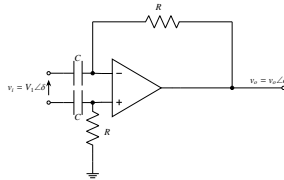


Fig. 13: Circuit diagram with capacitors, resistors, and an op-amp

- a) 0 b) π c) $\frac{\pi}{2}$ d) $-\frac{\pi}{2}$